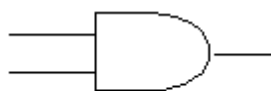



## Summary of Logic Gates

AND



A	B	$A \bullet B$
0	0	0
0	1	0
1	0	0
1	1	1

OR

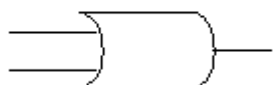


A	B	$A + B$
0	0	0
0	1	1
1	0	1
1	1	1

NOT




A	$\bar{A}$
0	1
1	0

NAND

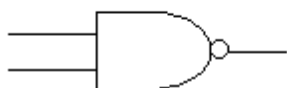

A	B	$\overline{(A \bullet B)}$
0	0	1
0	1	1
1	0	1
1	1	0

NOR

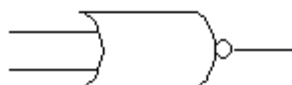

A	B	$\overline{(A + B)}$
0	0	1
0	1	0
1	0	0
1	1	0

XOR



A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

XNOR



A	B	$\overline{(A \oplus B)}$
0	0	1
0	1	0
1	0	0
1	1	1